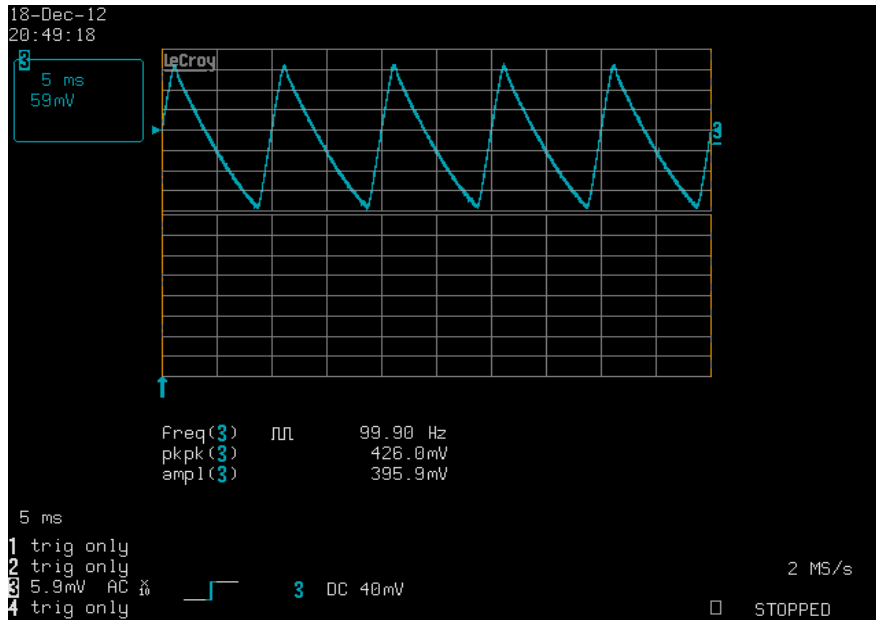



## CLC filtering

Ripple after rectifier = 426mVpp




## CRC filtering

Ripple after rectifier = 340mVpp

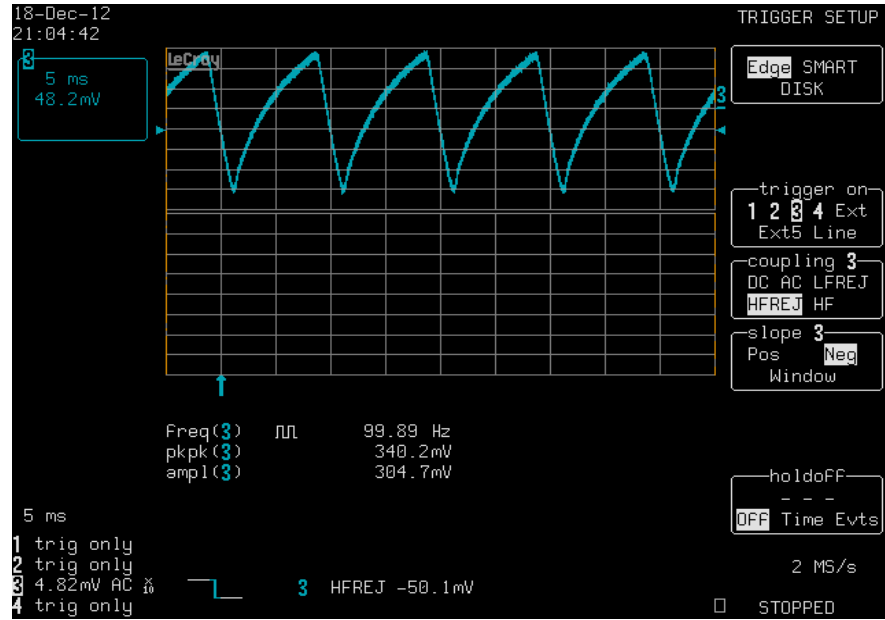

Ripple after 0.47mH coil = 4.5mVpp

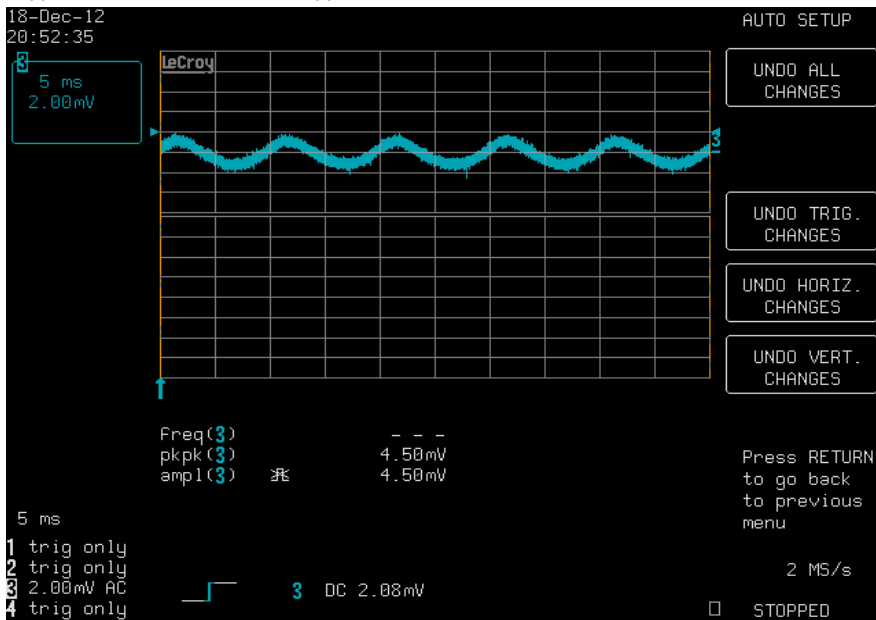

Ripple after Resistor = 98mVpp

